

### **LED:**

LED green 1 : PortB0

LED yellow 1 : PortB1

LED red1 : PortB2

LED green 2 : PortB3

LED yellow 2 : PortB4

LED red 2 : PortB5

All of them are also connected to Resistors which have value 330 Ohm

### **LCD:**

RS : PortD0

RW : GND

E : PortD1

D4 : PortD4

D5 : PortD5

D6 : PortD6

D7 : PortD7

### **74hc595 (expand connection pins to control 7-segment leds):**

SH\_SP : PortC0

DS ( first 74hc595 receives data) : PortC1, the others will connect to Q7 of the nearby

ST\_CP : PortC2

Data will be transfered through Q7 to DS of each 74hc595

### **7-segment LEDs:**

Each of leds will connect from Q0 to Q5 of 74hc595

### **Buttons:**

Button1: PortD2 (INT0)

Button2: PortD3 (INT1)

5V regulator : supply 5V for ATmega328, LCD and 74hc595

2.2V regulator : supply 2.2V for buttons, LEDs and 7-segment leds

Flow chart :

